

[Total No. of Questions - 9] [Total No. of Printed Pages - 2]
(2123)

1497

MCA 1st Semester Examination

Digital Organization (O.S.)

MCA-102

Time : 3 Hours

Max. Marks : 60

The candidates shall limit their answers precisely within the answer-book (40 pages) issued to them and no supplementary/continuation sheet will be issued.

Note : Attempt five questions in all, selecting one question from each section. Question 9 is compulsory.

SECTION - A

1. (a) What are the alpha numeric codes? Explain.
(b) $(AA1)_{16}$ to $(\text{-----})_{10}$, $(\text{-----})_8$
(c) $(63718)_{10}$ to $(\text{-----})_2$, $(\text{-----})_8$, $(\text{-----})_{16}$
(d) $(0.62652)_{10}$ to $(\text{-----})_2$, $(\text{-----})_8$ (12)
2. (a) $278+978$ using BCD addition.
(b) $110101 - 110111$ using 1's complement.
(c) $52.79 - 78.58$ using 9's complement.
(d) $(57)_8 + (65)_8$ using octal addition. (12)

SECTION - B

3. (a) Explain the working of BJT as a switch. Give Details of saturated & non-saturated logic. (12)
4. Draw & Explain the characteristics of ECL & CMOS. (12)

1497/20

[P.T.O.]

SECTION - C

5. Design all the basic gates using universal gates. Give four laws of Boolean algebra. (12)
6. Minimize the following using k-map & give your result in both SOP & POS forms.
- $F(w, x, y, z) = \Sigma(1, 4, 6, 7, 8, 9, 10, 11, 15)$ (12)

SECTION - D

7. Explain the working of BCD adder with neat & clean diagram. (12)
8. Design the JK flip flop using T-flip flop. Give applications of T-flipflop. (12)

SECTION - E

9. Write Technical note on the following:
- (a) Successive approximation method.
 - (b) Encoders.
 - (c) Depletion region in P-N Junction diode. (3×4=12)