

[Total No. of Questions - 9] [Total No. of Printed Pages - 2]
(2123)

1399

B. Tech 5th Semester Examination
Electrical Drives and Fact Devices (O.S.)
EE-5003

Time : 3 Hours

Max. Marks : 100

The candidates shall limit their answers precisely within the answer-book (40 pages) issued to them and no supplementary/continuation sheet will be issued.

Note : All the questions carry equal marks. Attempt five questions in total while selecting one question each from section A, B, C and D. Section E is compulsory. Answers to the questions should be precise and to the point.

SECTION - A

1. (a) What are the advantages of electrical drive over mechanical drive? **(5)**
(b) Explain the status of DC and AC drive. **(5)**
(c) Briefly classify the power modulators. **(10)**
2. (a) Explain voltage fed current regulated inverter drive with torque and flux control of induction motor. **(10)**
(b) Explain the different control strategies employed for synchronous motor drive. **(10)**

SECTION - B

3. (a) What are the applications of cyclo converter? What are the effects of load inductance on the performance of cyclo converter? **(10)**
(b) Explain the voltage control of single phase inverter with the help of wave forms. **(10)**
4. (a) Explain the 1-phase bridge voltage source converter. **(10)**

1399/900

[P.T.O.]

- (b) Describe the fundamental and harmonic voltages for a 1-phase bridge converter.

SECTION - C

5. (a) Why transmission interconnections are necessary and what are the major constraints of today's power system? (10)
- (b) Can FACTS technology provide solutions to the above constraints, if so discuss them in detail. (10)
6. (a) What are the series compensation schemes available using thyristor? (10)
- (b) Describe the principle of operation of thyristor controlled series compensator (TCSC). (10)

SECTION - D

7. (a) Explain TCR-FC (Thyristor Controlled Reactor with Fixed Capacitor) in transient state reactive power compensations. (10)
- (b) Explain the different types of reactive power characteristics. (10)
8. Explain the need of Electrical Breaking? What are the types of electrical breaking? Explain in detail. (20)

SECTION - E

9. (i) In SPWM for power factor improvement, Derive the following:
- (a) displacement angle (3)
- (b) supply power factor (3)
- (c) displacement factor (3)
- (d) harmonic factor (3)
- (ii) What do you understand by synchronous load? Explain. (3)
- (iii) Explain the application of drives in textile mills and its characteristics. (3)
- (iv) Describe the efficiency optimization control by flux program of induction motor drive. (2)