

[Total No. of Questions - 9]  
(2123)

[Total No. of Printed Pages - 3]

1407

B. Tech 5th Semester Examination

Industrial Electronics

EC-5004

Time : 3 Hours

Max. Marks : 100

*The candidates shall limit their answers precisely within the answer-book (40 pages) issued to them and no supplementary/continuation sheet will be issued.*

**Note :** Attempt any five questions in all by selecting at least one question from each of the section A, B, C, D and question 9th of Section E, which is compulsory. All questions carry equal marks.

#### SECTION - A

1. (a) Define the terms 'recombination time' and 'turn off time' of a thyristor. Explain the process of turn-off of a thyristor.  
(12)  
(b) A resonant pulse commutation circuit has a capacitor with  $C = 25\mu\text{F}$  and inductance  $L = 5\mu\text{H}$ . The initial capacitor voltage  $V_c(0) = 220\text{ V}$ . Find the circuit turn-off time, if the load current is 60A.  
(8)
2. Explain (a) Power MOSFETS (b) Series and Parallel Operation of Thyristors (c) Diac  
(20)

#### SECTION - B

- 3 (a) Draw the wave forms of a three-phase half-controlled bridge rectifier. Explain its operation with a circuit diagram.  
(12)

1407/1600

[P.T.O.]

- (b) For a full wave controlled rectifier the firing angle is  $60^\circ$  and the, input voltage  $v = 100 \sin 200t$ . Calculate the rms and average output voltages. (8)
4. Explain operation single phase half wave and full wave converter with RL load. Draw the necessary waveforms. (20)

### SECTION - C

5. (a) A dc chopper has a resistive load of  $20\Omega$  and input voltage  $V_s = 230$  V. When the chopper is ON, its voltage drop is 1.5 V and chopping frequency is 15 KHz. If the duty cycle is 80%, find the average output voltage and the chopper on time. (9)
- (b) Explain with the help of a circuit diagram and waveforms, the operation of a single-phase cyclo-converter using a center-tap transformer. (11)
6. (a) Explain how constant torque and constant power operation can be obtained from a separately excited DC motor using a solid-state converter, for a wide range of speed. (10)
- (b) Differentiate between voltage source and current source induction motor drives for speed control. (10)

### SECTION - D

7. (a) Explain switched mode power supply. Discuss in detail step up and step down circuits for switched mode power supplies. (10)
- (b) Explain in detail integrated circuits for switched mode regulators. (10)
8. Explain (a) Induction heating and its applications (b) Dielectric Heating and its applications. (20)

**SECTION - E**

9. (a) In Triacs which of the modes the sensitivity of gate is high.
- (b) Define the term pinch off voltage of MOSFET.
- (c) Under what conditions a single phase fully controlled converter gets operated as an inverter.
- (d) State the principle of phase control in AC-DC converters.
- (e) Define the term duty cycle in DC-DC converters.
- (f) What is a DC chopper?
- (g) Define the term Inverter gain.
- (h) Differentiate between single phase and three phase rectifiers.
- (i) Explain two factors on which the load voltage of a D.C. chopper circuit depends.
- (j) What is basic principle of a switched mode power supply?  
**(2×10=20)**