

[Total No. of Questions - 9]  
(2063)

[Total No. of Printed Pages - 4]

830

B.Tech 4th Semester Examination

Electronic Logic Circuit Design

EC-4003

Time : 3 Hours

Max. Marks : 100

*The candidates shall limit their answers precisely within the answer-book (40 pages) issued to them and no supplementary/continuation sheet will be issued.*

**Note :** Attempt five questions in all, selecting one question each from sections A, B, C and D. Section - E is compulsory.

**SECTION - A**

1. (a) Design a 4 bit binary to grey code converter.  
(b) Design a direct logic circuit to generate the sequences 100111 and 011101 simultaneously. **(10,10)**
2. (a) What do you mean by race around condition? How it is removed? Explain the working of positive edge triggered master-slave JK flip flop. Explain its excitation table.  
(b) Differentiate between synchronous and asynchronous circuits. Explain the various classifications of switching circuits. **(12,8)**

830/2000

[P.T.O.]

**SECTION - B**

3. (a) Draw a two input, two output synchronous sequential circuit which examines the input sequence in non- overlapping strings of three inputs each and produces a one output coincident with the last input of the string if and only if the string consisted of either 2 or 3 1's. Use S-R flip-flop in your realization.
- (b) What do you mean by the cascading of ripple counters? Design a 3-bit ripple counter. Explain the effects of propagation delay in ripple counters. For what minimum value of propagation delay in each FF will a 10-bit ripple counter skip a count when it is clocked at 10MHz. **(10,10)**
4. (a) Design a universal shift register with flip flops.
- (b) Design a JK counter that goes through states 2, 4, 5, 7, 9, 10, 12, 2, 4, 5..... Is the counter self- starting? Modify the circuit such that whenever it goes to any invalid state it comes back to state 2. **(10,10)**

**SECTION - C**

5. (a) A sequential circuit has two pulse inputs,  $x_1$  and  $x_2$ . The output of the circuit becomes 1 when one or more consecutive  $x_1$  pulses are followed by two  $x_2$  pulses. The output then remains 1 for all subsequent  $x_2$  pulses until an  $x_1$  pulse occurs.

- (a) Derive a minimal state table describing the circuit operation.
  - (b) Synthesize the circuit using set-reset flip-flops. (20)
6. A sequential circuit has two inputs  $x_1$  and  $x_2$  and two outputs  $z_1$  and  $z_2$ , is to be designed so that  $z_i$  (for  $i=1, 2$ ) takes on the value 1 if and only if  $x_i$  was the input that changed last.
- (a) Find a minimum-row reduced flow table and a valid assignment.
  - (b) Assuming that all inputs are available in an uncomplemented as well as complemented form, show a realization using NAND gates. (20)

#### SECTION - D

7. Design a hazard free asynchronous sequential circuit with two input  $x_1$  and  $x_2$  and two outputs  $G$  and  $R$ , which is to behave in the following manner. Initially, both input and both outputs are equal to 0. Whenever  $G = 0$  and either  $x_1$  or  $x_2$  becomes 1,  $G$  turns on i.e. becomes 1. When the second input becomes 1,  $R$  turns on. The first input that changes from 1 to 0 turns  $G$  off.  $R$  turns off when  $G$  is off and either input changes from 1 to 0. (20)
8. (a) Write a short note on hazards. Explain the methods to design hazard free combinational networks.

[P.T.O.]

- (b) What are types of decomposition? What are the conditions for serial and parallel decomposition? (10,10)

### SECTION - E

9. (a) Realize the given T flip flop in such a way that it acts as a D flip flop.
- (b) Convert a D-FF into JK-FF.
- (c) Design a 3-bit ring counter.
- (d) What are the limitations of finite state machine?
- (e) Tabulate the excitation tables of JK and SR flip flop.
- (f) With the help of example explain the term glitch.
- (g) Write the following function in standard SOP
- $$F(x, y, z) = xy + z$$
- (h) What are pulse mode circuits?
- (i) Write the differences between Mealy and Moore type machines.
- (j) Explain the difference between latch and flip flop. (2×10=20)