

[Total No. of Questions - 9] [Total No. of Printed Pages - 3]  
(2064)

14677

**B. Tech 4th Semester Examination**  
**Network Analysis & Synthesis (O.S.)**  
**EC-4004**

**Time : 3 Hours**

**Max. Marks : 100**

*The candidates shall limit their answers precisely within the answer-book (40 pages) issued to them and no supplementary/continuation sheet will be issued.*

- Note :** (i) Section E is compulsory.  
(ii) Attempt other four sections selecting one from each section A, B, C and D.

**SECTION - A**

1. A voltage  $v = 300 \sin 314t$  is applied at  $t = 2.14$  msec to a series R-C circuit having resistance  $10\Omega$  and capacitance  $200\mu\text{F}$ . Find an expression for current. Also, find the value of current 1msec after switching on. (20)
2. In the circuit of Fig. 1,  $S_1$  is closed at  $t = 0$  and  $S_2$  is opened at  $t = 4$  msec. Determine  $i(t)$  for  $t > 0$  (assume inductor is initially de-energised) (20)

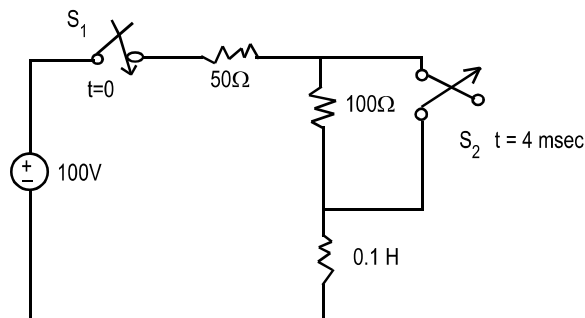


Fig. 1

14677/800

[P.T.O.]

## SECTION - B

3. Discuss poles and zeros of network function and hence obtain pole-zero location for the function

$$p(s) = \frac{(2s + 4)(s + 4)}{s(s + 1)(s + 3)} \quad (20)$$

4. (a) Explain the necessary conditions for driving point immittance function and transfer function. (10)
- (b) Check the stability of the system with characteristics equation  $s^5 + 4s^4 + 8s^3 + 8s^2 + 7s + 4 = 0$ . (10)

## SECTION - C

5. For the network shown in Fig. 2, determine

(a) tie-set matrix.

(b) Loop impedance matrix

(c) Loop currents.

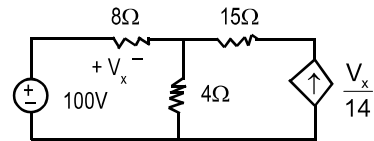


Fig. 2

(20)

6. Find the short circuit and open circuit impedances of the network shown in Fig. (3) and hence obtain its  $\pi$  equivalent. (20)

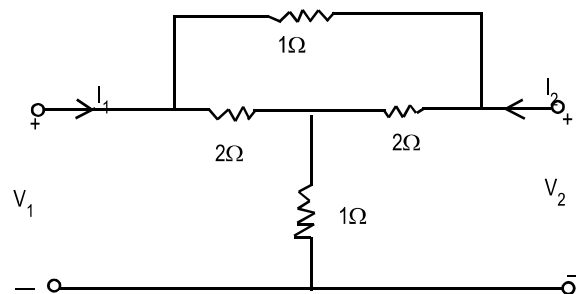


Fig. 3

## SECTION - D

7. Explain the significance of passive filter alongwith a performance parameters. Discuss the performance parameters of constant-K high pass filters. (20)
8. Write down the properties of a positive real function and hence determine whether the function

$$p(s) = \frac{2s^2 + 5}{s(s^2 + 1)} \text{ is positive real or not} \quad (20)$$

## SECTION - E

9. (i) What is Hurwitz function? List its properties.

- (ii) Find the hybrid parameters of the network shown in Fig. 4.

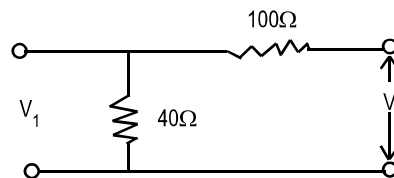


Fig. 4

- (iii) Explain Routh Hurwitz stability criteria with suitable example.

- (iv) Synthesize the network if

$$z(s) = \frac{s^5 + 5s^3 + 4s}{s^4 + 3s^2 + 1} \text{ as caner-I form}$$

- (v) Define the following with examples.

(a) Fundamental cut-set matrix

(b) Fundamental tie-set matrix

(c) Twigs

(d) Links

(5×4=20)