

[Total No. of Questions - 9] [Total No. of Printed Pages - 4]
(2123)

1339

B. Tech 3rd Semester Examination
Analog Electronics Engineering (N.S.)
EC-212

Time : 3 Hours

Max. Marks : 100

The candidates shall limit their answers precisely within the answer-book (40 pages) issued to them and no supplementary/continuation sheet will be issued.

- Note :** (i) Attempt five questions in all, select one question from each sections A, B, C and D. Section E is compulsory.
(ii) Assume suitable data if necessary.

SECTION - A

1. (a) Describe the low frequency & small signal analysis of CE configuration of a transistor amplifier and derive the equations for the following:
- (a) Current gain (A_i)
 - (b) Voltage gain (A_v)
 - (c) Power gain (A_p)
 - (d) Input impedance (Z_i)
 - (e) Output impedance (Z_o)
 - (f) Output admittance (Y_o) **(10)**
- (b) Calculate Current gain (A_i), Voltage gain (A_v), Power gain (A_p), Input impedance (Z_i), Output impedance (Z_o) for CE amplifier design with source internal resistance 800 ohms

1339/1200

[P.T.O.]

and it is terminated with load resistance of 2 kilo ohms.
 Let $h_{ie} = 1100$ ohms, $h_{fe} = 50$, $h_{re} = 2.5 \times 10^{-4}$, $h_{oe} = 24 \times 10^{-6}$ A/V. **(10)**

2. (a) Derive the formula for higher cut-off frequency and lower cut-off frequency of multi-stage amplifier circuit where N number of identical & non-interacting stages are cascaded. **(10)**
- (b) Compare the coupling techniques used for cascading of multi stage amplifier along with their merits and demerits. Also list the application where the coupling techniques are used. **(10)**

SECTION - B

3. (a) Why hybrid model is used for transistor? Draw the hybrid Π model at low frequency and high frequency for an CE amplifier. **(10)**
- (b) Derive an expression for high frequency current gain with resistive load for an amplifier. **(10)**
4. (a) Explain class A, class B, class AB and push-pull amplifier operation with their advantages, disadvantages and applications. **(10)**
- (b) What do you understand by distortion in large signal amplifier and how is it calculated for class A, class B, class AB amplifier? **(10)**

SECTION - C

5. (a) Draw and explain the operation of a tuned amplifier circuit. Draw its equivalent cascade pair representation. Also draw y-parameter two port model for the same and define the y-parameter. **(10)**
- (b) Derive an expression for the efficiency of Class C amplifier. **(10)**

6. (a) Discuss in detail the effects of negative voltage series feedback on the performance parameters of an amplifier? (10)
- (b) What do you understand by tuned amplifier and discuss the merits and demerits of single and double tuned amplifier. (10)

SECTION - D

7. (a) Derive an expression for the frequency of oscillation of Hartley Oscillator. (10)
- (b) What is need of voltage regulator in electronic circuit? Describe the OP AMP based voltage regulator. (10)
8. (a) Derive an expression for the frequency of oscillation of Colpitts Oscillator. (10)
- (b) How will you differentiate between voltage regulator and voltage? Describe the Zener diode based voltage regulator. (10)

SECTION - E

9. Answer the following precisely:
- (i) Compare CE, CC, and CB configuration of BJT.
- (ii) Derive the equation of transconductance of CASCADE amplifier.
- (iii) What are the advantages and disadvantages of increasing emitter resistance (R_e)?
- (iv) In the miller's theorem, if the series impedance Z connected between input & output terminals of a network happens to be a capacitor, then what will happen to the miller components?

[P.T.O.]

- (v) Compare series and shunt amplifier.
- (vi) Write down advantage & disadvantage of positive feedback.
- (vii) Draw the circuit diagram of RC coupled phase shift oscillator & write the equation of its frequency of operation.
- (viii) Define load regulation & line regulation.
- (ix) Draw the circuit diagram of RC coupled amplifier.
- (x) Write short note on IC regulator. **(2×10=20)**