

[Total No. of Questions - 9] [Total No. of Printed Pages - 4]
(2123)

1340

B. Tech 3rd Semester Examination

Circuit Theory and Network Analysis & Synthesis (N.S.)

EC-213

Time : 3 Hours


Max. Marks : 100

The candidates shall limit their answers precisely within the answer-book (40 pages) issued to them and no supplementary/continuation sheet will be issued.


Note : Attempt five questions in all, select one question from each sections A, B, C and D. Section E is compulsory.

SECTION - A

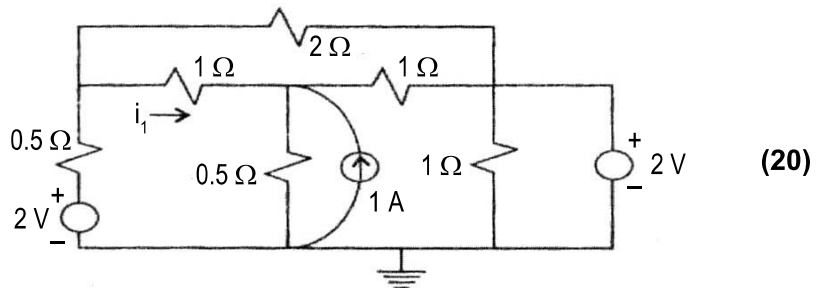1. For the circuit shown below find the numerical value of current i_1 using nodal analysis method.



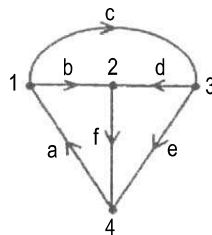2. For the graph shown in the given figure, Find the



- (i) Twigs (ii) Links
(iii) Fundamental cutset (iv) Fundamental loop

1340/1200

(20)
[P.T.O.]

SECTION - B

3. The response of a system to an impulse is given by

$$h(t) = 0.18 [\exp(-0.32t) - \exp(-2.1t)]$$


Find the response of the system to the unit step function. (20)

4. In a series RLC circuit, $R = 2 \text{ k}\Omega$, $L = 1 \text{ mH}$, and $C = 1/400 \text{ }\mu\text{F}$. If a voltage of 100V is applied across the series combination then determine the


(i) Resonant frequency (ii) Q factor (iii) Half power frequencies (20)

SECTION - C

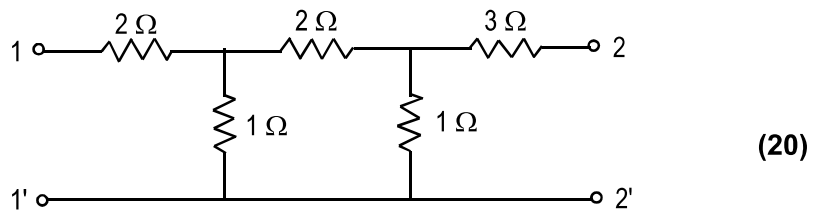5. Find the admittance parameters of the two-port network in the figure shown below.



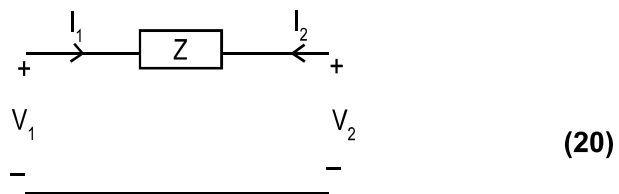6. Find the hybrid parameters of the two-port network in the figure shown below.



SECTION - D

7. Check the positive realness of the following function?


$$\frac{s^2 + s + 6}{s^2 + s + 1} \quad (20)$$

8. A designer require to synthesize a network with the following data:
- Impedance function has simple poles at -2 & -6 .
 - Impedance function has simple zeros at -3 & -7 .
 - $Z(0) = 20$


Is it possible to synthesize it? Give reasons. Hence find one Cauer-I & Foster-I Representations. **(20)**

SECTION - E

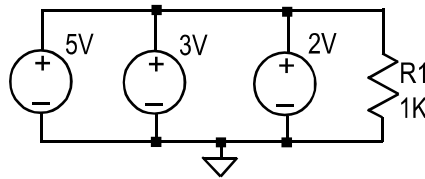9. (a) Kirchoff s law is applicable for linear as well as non linear circuits? Justify your answer by taking a suitable example.
- (b) What is V_o across resistance $R_1 = 1K\Omega$ if all the voltage sources are ideal in the circuit shown?



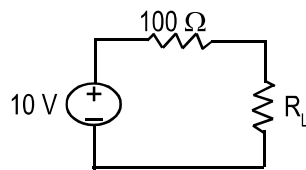- (c) Find the maximum power that can be transferred to the load resistor R_L from the voltage source in the figure shown below?



- (d) The Laplace transform of $i(t)$ is given by

$$I(s) = \frac{2}{s(1+s)}$$

At $t \rightarrow \infty$ the value of $i(t)$ tends to?

[P.T.O.]

- (e) A series RLC circuit has a resonance frequency of 1 KHz and a quality factor $Q = 100$. If each of R, L and C is doubled from its original value, then what is the new Q of the circuit?
- (f) What is the significance of Q factor?
- (g) Why there is need of the analysis of two port networks using various parameters?
- (h) What is the condition of reciprocity in Z-parameters?
- (i) State necessary and sufficient condition for positive real functions (prf).
- (j) Test whether the following polynomial is Hurwitz.

$$s^4 + 7s^3 + 6s^2 + 21s + 8$$

(2×10=20)