

Time : 3 Hours

Max. Marks : 100

The candidates shall limit their answers precisely within the answer-book (40 pages) issued to them and no supplementary/continuation sheet will be issued.

Note : Section E is Compulsory. Attempt other four questions, selecting one from each section A, B, C, D.

SECTION - A

- Steady state conditions exist at $t=0(-)$ and switch S is closed at $t=0$ in Fig. 1. Find $i_a(t)$ and $i_b(t)$. Using Laplace Transform. (20)

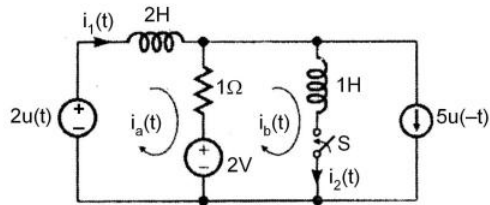


Fig. 1

- Explain:

- Three types of systems
- Special Signals
- Butterworth polynomial
- Frequency normalization

(20)

[P.T.O.]

SECTION - B

- For the network shown in Fig. 2, calculate Y and T parameters with 3Ω load across port 2. (20)

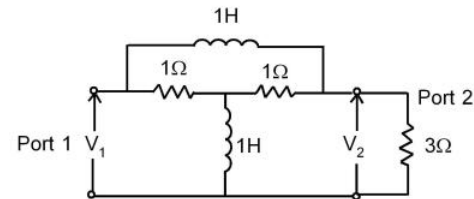


Fig. 2

- Justify Norton theorem as converse of Thevenin theorem. Find I_1 and I_2 in the circuit shown in Fig. 3. Use superposition principle. (20)

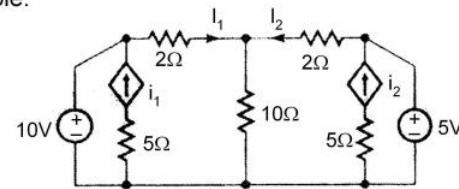


Fig. 3

SECTION - C

- Explain cut set and tie set matrix with example. Develop fundamental cut-set matrix of the network shown in Fig. 4. (20)

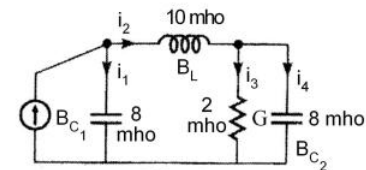


Fig. 4

- Test whether the polynomial $P(s) = s^7 + 2s^6 + 2s^5 + s^4 + 4s^3 + 8s^2 + 8s + 4$ is Hurwitz or not. Also explain properties of Hurwitz polynomial. (20)

SECTION - D

7. Design a prototype constant-K band pass filter having cut-off frequencies of 4 KHz and 6 KHz and a nominal impedance of 628Ω . (20)
8. Synthesize $F(s) = \frac{4(s+1)(s+3)}{s(s+2)}$ using Cauer I and Cauer II form of realization when $F(s)$ is either an impedance or admittance. (20)

SECTION - E

9. (a) Test whether $\frac{s+a}{s^2+bs+c}$ is PRF.
 (b) What is a routh criterion?
 (c) In series RLC circuit, determine value of R for critical damping, assume $L=2$ H, $C=5$ μ F.
 (d) What is driving point impedance function?
 (e) What is significance of poles and zeroes?
 (f) What is characteristic impedance?
 (g) For $V(s) = \frac{(s+2)}{s(s+1)}$, the initial and final values of $v(t)$.
 (h) When superposition theorem is applied to a circuit, how does the dependent voltage source behave?
 (i) Show the effect of increasing the filter order on the characteristic frequency response of a Butterworth low Pass filter.
 (j) What are the properties of incidence matrix?
 (10 \times 2=20)