

[Total No. of Questions - 9] [Total No. of Printed Pages - 4]
(2125)

15110

B. Tech 4th Semester Examination
Power Electronics (OS)
EE-4004

Time : 3 Hours

Max. Marks : 100

The candidates shall limit their answers precisely within the answer-book (40 pages) issued to them and no supplementary/continuation sheet will be issued.

Note : Attempt five questions in all, selecting one question from each of the section A, B, C and D and all the subparts of the question in Section E.

SECTION - A

1. (a) What is meant by ratings and protections of thyristors? Discuss different ratings and protection schemes of an SCR. (10)
- (b) Latching current for an SCR inserted in between a dc voltage source of 200 V and load is 100 mA. Calculate the minimum width of gate-pulse current required to turn on this SCR in case load consists of 0.2 H inductance. (10)
2. What are the main features of firing circuits? Give detailed explanations of the resistance firing circuit. What are its advantages and limitations? (20)

SECTION - B

3. (a) What is an ac voltage controller? List some of its industrial applications. Enumerate its merits and demerits. (10)

2

15110

- (b) A single phase voltage controller feeds power to a resistive load of 3 ohms from 230 V, 50 Hz source. Calculate the maximum values of average and rms thyristor's currents for any firing angle α . (10)
4. (a) A single phase half wave SCR circuit feeds power to a resistive load. Draw waveforms for source voltage, load voltage, load current and voltage across the SCR for a given firing angle α . Hence obtain expressions for average and rms load voltages in terms of source voltage and firing angle. (10)
- (b) A single-phase full converter feeds power to RLE load with $R=6$ ohms, $L=6$ mH and $E = 60$ V. The ac source voltage is 230 V, 50 Hz. For continuous conduction, find the average value of load current for a firing angle delay of 50° (10)

SECTION - C

5. (a) What are line commutated inverters? How do they operate? Explain the difference between line commutated and force commutated inverters. (10)
- (b) A single-phase full bridge inverter is connected to an R.L. Load. For a dc source voltage of V_s , and output frequency $f=1/T$, obtain expressions for load current as a function of time for the first two half cycles of the output voltage. (10)
6. (a) Explain the mechanism of operation of a thyristorised three phase half bridge inverter. (10)
- (b) How does a three-phase series inverter function? (10)

[P.T.O.]

3

15110

SECTION - D

7. (a) Discuss the principle of dc chopper operation. Derive an expression for its average dc output voltage. (10)
- (b) A dc battery is charged from a constant dc source of 220 V through chopper. The dc battery is to be charged from its internal emf of 90 V to 122 V. The battery has internal resistance of 1 ohm. For a constant charging current of 10 A, compute the range of duty cycle. (10)
8. (a) What is a cycloconverter? Enumerate some of its industrial applications. (10)
- (b) What is the difference between the operation of the three phase three pulse cycloconverter with R load and RL load? (10)

SECTION - E

9. Answer the following questions.
- (a) State the functions of the gate of a thyristor.
- (b) Write the expression of output voltage for a single phase voltage regulator.
- (c) For 3-phase full wave converter, write the expression for its output voltage in terms of supply voltage, source inductance, load current etc.
- (d) What is the function of snubber circuit connected across SCR?
- (e) What is the sequence of the total number of SCRs conducting simultaneously in a 3-phase full converter with overlap considered?

[P.T.O.]

4

15110

- (f) A single phase bridge inverter delivers power to a series connected RLC load with $R=2$ ohms, $\omega L=8$ ohms. For this inverter load combination what is the magnitude of $1/\omega C$ in ohms for the load commutation to occur?
- (g) In single phase modulation of PWM inverters, what is the value of pulse width in degrees so that third harmonic can be eliminated?
- (h) How many thyristors are required for single-phase to single-phase cycloconverter of the mid-point type?
- (i) In dc choppers, if T_{on} is the on-period and f is the chopping frequency, and input voltage is V_s . Then write the expression for output voltage?
- (j) When anode is positive with respect to cathode in an SCR, the number of blocked P-N junctions is.....
(2×10=20)