

B. Tech 3rd Semester Examination

Circuit Theory and Network Analysis & Synthesis (NS)

EC-213

Time : 3 Hours


Max. Marks : 100

The candidates shall limit their answers precisely within the answer-book (40 pages) issued to them and no supplementary/continuation sheet will be issued.


Note : Attempt five questions in all, selecting one question from each sections A, B, C and D. Section E is compulsory.

SECTION - A

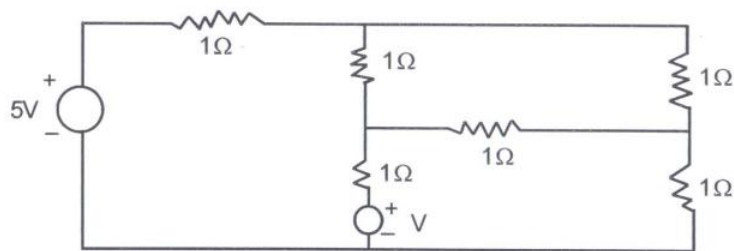1. In the following circuit find V by mesh method such that the current through the 5V source is zero. (20)



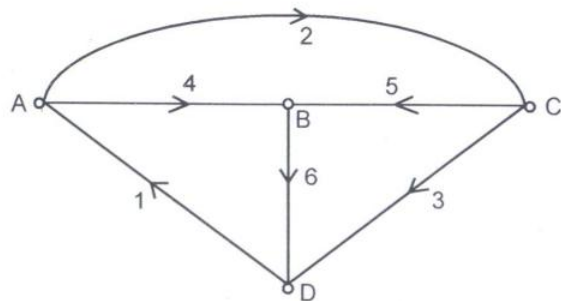2. Find the number of possible trees of the graph shown in Fig. below. (20)




SECTION - B

3. Determine the Inverse Laplace transform of

$$\frac{s+4}{2s^2+5s+3} \quad (20)$$

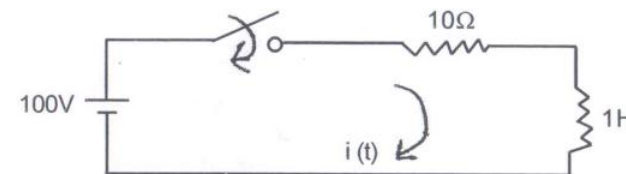4. In the given network of following figure the switch is closed at $t=0$ with zero current in the inductor find


$$i, \frac{di}{dt}, \frac{d^2i}{dt^2} \text{ at } t = 0^+ \quad (20)$$



SECTION - C

5. Express z parameters in terms of y parameters. (20)

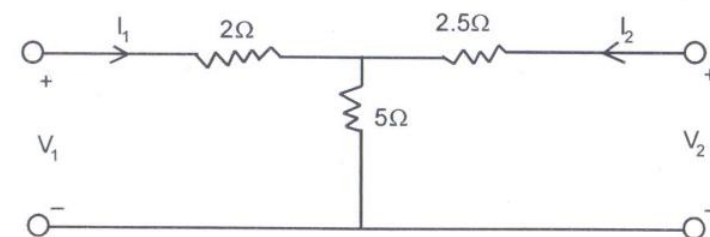6. Find the equivalent π network shown in figure below. (20)



SECTION - D

7. Test whether the polynomials

(i) $P(s) = s^4 + s^3 + 3s^2 + 2s + 12$

(ii) $P(s) = s^4 + s^3 + 5s^2 + 3s + 4$

are Hurwitz?


(20)

8. Realize cover form of following LC impedance function

$$Z(s) = \frac{10s^4 + 12s^2 + 1}{2s^3 + 2s} \quad (20)$$

SECTION - E

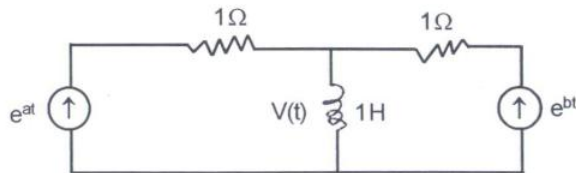9. (a) Define Kirchoff's Current Law (KCL) and Kirchoff's Voltage Law (KVL).
- (b) State Superposition Theorem.
- (c) The number of independent loops for a network with n nodes and b branches is
 (i) $n-1$ (ii) $b-n$ (iii) $b-n+1$
 (iv) Independent of number of nodes.
- (d) What are the advantages of Laplace transform method?
- (e) In hybrid parameter what is short circuit input impedance and what is short circuit forward current gain?
- (f) Give any two properties of positive real function.
- (g) Function $F(s) = \frac{s+3}{s+1}$. Find its pole and zero.
- (h) What do you mean by causality in synthesis procedure?
- (i) What is half power and cutoff frequency?
- (j) In the circuit below the voltage $V(t)$ is



- (i) $e^{at} - e^{bt}$ (ii) $e^{at} + e^{bt}$ (iii) $ae^{at} - be^{bt}$ (iv) $ae^{at} + be^{bt}$

(2×10=20)