

[Total No. of Questions - 9] [Total No. of Printed Pages - 4]  
(2123)

1367

B. Tech 3rd Semester Examination

Circuit Theory (O.S.)

EE(ID)-3001

Time : 3 Hours

Max. Marks : 100

The candidates shall limit their answers precisely within the answer-book (40 pages) issued to them and no supplementary/continuation sheet will be issued.

**Note :** Attempt five questions in all, by selecting atleast one question from each of sections A, B, C and D, question no. 9 of section E, which is compulsory. All questions carry equal marks.

**SECTION - A**

1. (a) A half cycle sine wave function is given by  $v(t)=\sin wt$ . Determine its Laplace transform.
- (b) In Fig. 1, the battery voltage is applied for a steady state period. Obtain the complete expression for the circuit after closing the switch K. (20)

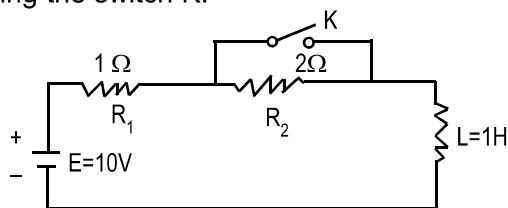


Fig. 1

2. A voltage wave is shown in Fig. 2.
  - (a) Find exponential Fourier series for the wave.

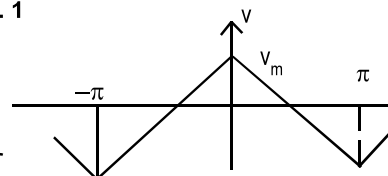


Fig. 2

1367/1100

[P.T.O.]

- (b) If this wave is applied to a series combination of resistance (R) and capacitor (C) find current.
- (c) Find power and power factor of the circuit. **(20)**

**SECTION - B**

3. Obtain I and II equivalent circuits for the network of Fig. 3 by using impedance and admittance parameters respectively. **(20)**

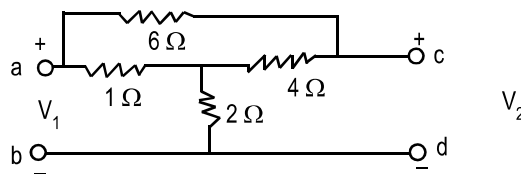


Fig. 3

- 4. (a) Derive the condition of reciprocity and symmetry in h-parameter network.
- (b) Find the y-parameters for the network of Fig. 4. **(20)**

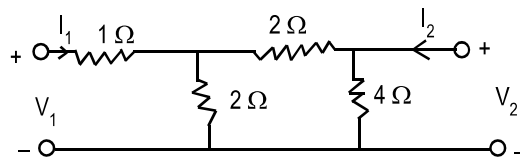


Fig. 4

**SECTION - C**

5. Fig. 5 represents a resistive network. Determine the numbers of branches, number of nodes and links. Write down the incidence matrix for the given network. Also develop the network equilibrium equation. **(20)**

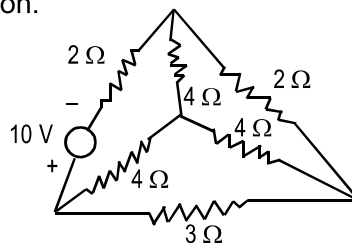


Fig. 5

6. (a) Write the loop equations in time domain and s domain, if  $L_1=L_2=2H$ ,  $V_1=5 \sin wt$ ,  $V_2=5 \sin (wt+30^\circ)$   
 $M=10H$  for the circuit of Fig. 6.

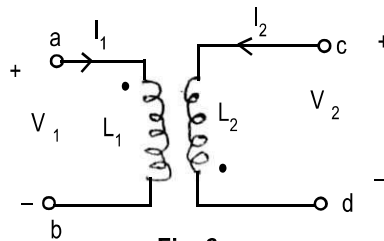


Fig. 6

- (b) For an ideal transforming find the input impedance. Assume load impedance to be  $Z_2$ . (20)

#### SECTION - D

7. Check whether the following function is Hurwitz

(a)  $s^5 + 14s^4 + 48s^3 + 200s^2 + 500s + 200 = 0$

- (b) Represent  $z(s) = \frac{s^4 + 7s^2 + 9}{s(s^2 + 4)}$  in the form of Cauer LC network (20)

8. (a) Driving point impedance of an LC network is given by

$$z(s) = \frac{10s^4 + 12s^2 + 1}{2s(s^2 + 1)}$$

determine the first foster form.

- (b) Find the second foster form of the admittance function given by

$$y(s) = \frac{s(s^2 + 9)}{10(s^2 + 4)(s^2 + 25)} \quad (20)$$

[P.T.O.]

**SECTION - E (Compulsory)**

9. (a) Find the Laplace transform of shifted step function.
- (b) Describe z and y parameters.
- (c) What is non-linear circuit? Can Ohm's law be applied to a non-linear circuit?
- (d) How can you obtain a fundamental Tie set matrix?
- (e) What is the importance of poles and zeros?
- (f) What is initial and final value theorems?
- (g) What is waveform symmetry?
- (h) What are properties of a transfer function?
- (i) Define co-efficient of coupling.
- (j) List four important properties of a driving point impedance function of an LC network. **(10×2=20)**