

[Total No. of Questions - 9] [Total No. of Printed Pages - 4]
(2123)

1336

B. Tech 3rd Semester Examination

Circuit Theory (N.S.)

EE-212

Time : 3 Hours


Max. Marks : 100

The candidates shall limit their answers precisely within the answer-book (40 pages) issued to them and no supplementary/continuation sheet will be issued.

Note : Attempt five questions from all selecting one question from each section A, B, C & D and all the subparts of the questions in section E.

SECTION - A

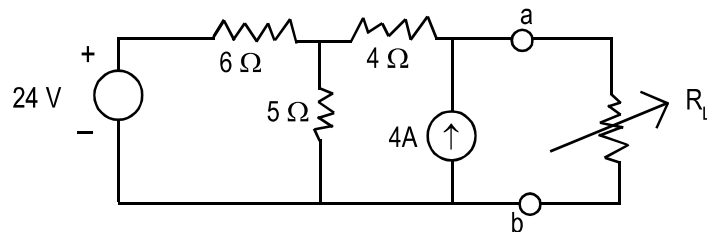1. (a) State and explain the Thevenin's theorem. Consider both the cases of dependent and independent sources. **(10)**
- (b) Determine the Thevenin equivalent circuit of the circuit given below to the left of the terminal ab. Find the current through R_L if $R_L = 6\Omega$. **(10)**




2. (a) Determine the Laplace transform of the following function
(i) Unit step function (ii) Unit ramp function, (iii) Unit impulse function. **(9)**

1336/1000


[P.T.O.]

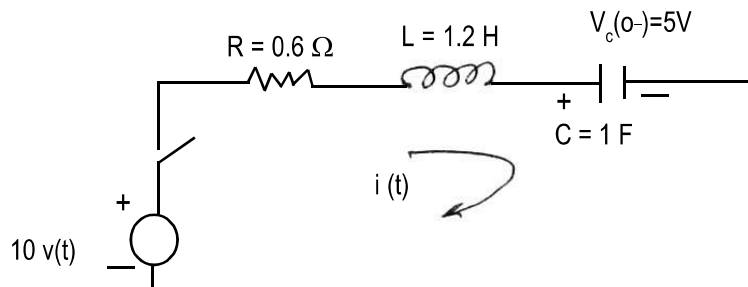- (b) In a series RLC network given below the initial voltage on the capacitor is 5V. Find $i(t)$ following switching of the circuit. Assume zero initial condition for the inductor and polarity of charge as shown in the figure. (11)



SECTION - B

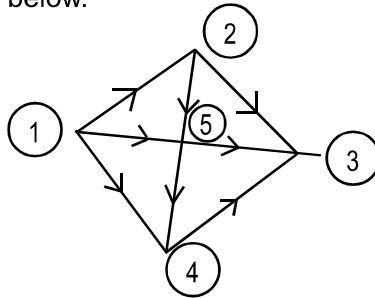3. (a) What are the properties of a tree in a graph? Explain the procedure for obtaining fundamental tie set and cut set matrix with an example. (12)
- (b) Obtain the tie set matrix and cut-set matrix for the graph shown below. (8)




4. (a) Define PR function. What are the properties of a P-R function? Explain the procedure of P-R function. (12)
- (b) Test the function for its positive realness.

$$Z(s) = \frac{s^3 + 6s^2 + 5s + 4}{s^3 + 2s^2 + 3s + 3} \quad (8)$$

SECTION - C

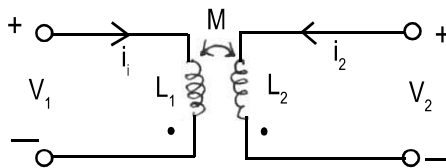
5. (a) A $15\ \mu\text{F}$ capacitor is connected through a $500\ \text{k}\Omega$ resistor to a dc source (10V). After being charged for half minute the capacitor is disconnected and discharged through a resistor (R). Determine the energy dissipated in R . (10)
- (b) Determine and derive an expression for the transient response of series R-C circuit with sinusoidal excitation. (10)
6. (a) Draw the time domain and frequency domain equivalent circuit of the following coupled circuit with the given dot convention. (8)



- (b) Two coupled coils have $K=0.3$, $N_1=400$ turns and $N_2=600$ turns. The mutual flux is being $0.6\ \text{Wb}$. Find the primary coil flux. If the primary current is 12A , find the primary coil inductance. Also determine the secondary inductance. (12)

SECTION - D

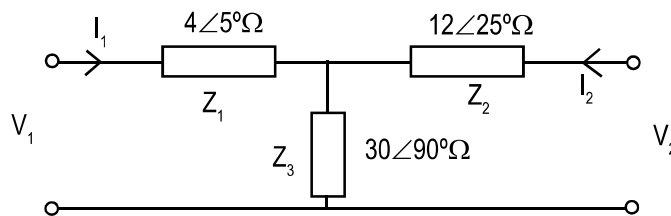
7. (a) Differentiate between one port, two port and n port network. (10)
- (b) Determine the Z-parameter for the following circuit. (10)



[P.T.O.]

8. (a) What are the ABCD parameters for a two port network? Prove that for a symmetric two port network $AD - BC = 1$.
(12)

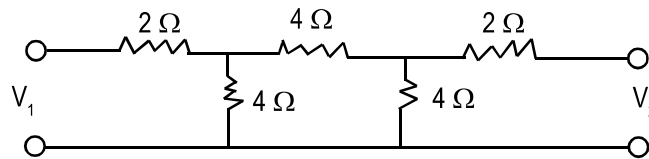- (b) Determine the ABCD parameters for the following network.
(8)



SECTION - E

9. (a) State superposition theorem.
 (b) Write the network equation for a series R-L circuit excited by step input in time domain and s-domain.
 (c) Define final value theorem.
 (d) Compare cut set and tie set matrix of a graph.
 (e) What do you mean by graph, subgraph, path and connected graph?
 (f) A function is given by $\frac{2s}{s+5}$. Draw pole zero plot.
 (g) What are the conditions for which a polynomial $P(s)$ is Hurwitz?
 (h) Calculate the time taken by a capacitor of $5\ \mu\text{F}$ in series with $200\ \text{k}\Omega$ resistance to be charged up to 70% of the final value.
 (i) Explain the condition of symmetry in Z parameter representation.
 (j) Express Z parameters in terms of ABCD parameters.
(2×10=20)