

Total No. of Questions - 8] [Total No. of Printed Pages - 3]
(2124)

1625

M. Tech 1st Semester Examination
Design of Electronics System

EC-102

Time : 3 Hours

Max. Marks : 100

The candidates shall limit their answers precisely within the answer-book (40 pages) issued to them and no supplementary/continuation sheet will be issued.

Note : (i) Assume suitable data wherever necessary.
(ii) Attempt Any FIVE Questions.

1. (a) Explain the successive approximation ADC with a suitable diagram. Compare dual slope ADC and successive approximation ADC in terms of accuracy conversion speed and resolution. What is the resolution of 12 bit successive approximation ADC? (12)
- (b) What do you mean by hazard free asynchronous sequential circuits? (6)
- (c) How many comparators are required to design 12-bit flash type ADC? (2)
2. (a) Implement the following Boolean function with only one 4X 1 MUX
 $F(A, B, C, D) = \sum m(0, 2, 3, 6, 8, 9, 12, 14)$ (10)
- (b) Design 24-bit comparator using six 7485 comparators in two levels. (10)

[P.T.O.]

3. (a) Explain the steps involved in programming of FPGA. (8)
- (b) List the application of P.L.A. (4)
- (c) Realize EX-OR gate using only four NAND gates. Also realize Full-Adder circuit using only NAND gates. (8)
4. (a) Design a BCD to Excess-3 code converter and implement using suitable P.L.A. (15)
- (b) Write the design procedure for synchronous counter. Also design MOD-5 ripple counter. (5)
5. (a) Carry out the following conversion:
 - (i) Convert a SR-latch to T Flip-Flop (10)
 - (ii) Convert JK to SR flip-Flop (10)
- (b) Draw and explain the clocked SR Flip-flop in detail. (5)
- (c) Write notes on bounce elimination switches. (5)
6. (a) Write the design procedure for asynchronous counter. Also design MOD-6 ripple counter. (8)
- (b) Analyze the sequential circuit as shown in Fig. 1. (12)

 


Fig. 1

7. (a) Explain the method to eliminate static hazards in asynchronous circuits with an example. (10)
- (b) Write notes on:
 - (i) Electromagnetic Interference and Electromagnetic compatibility. (10)
 - (ii) Grounding and shielding of digital circuits. (10)
- (a) Design a 3-bit binary UP/DOWN counter with a direction control M. Use JK flip-Flops. (8)
- (b) Design a clocked sequential circuit for state diagram as shown in Fig. 2. (Use state reduction technique). Use D flip-flop. (12)

 


Fig. 2