

SECTION - B

B. Tech 8th Semester Examination

Computer Applications to Power System Analysis (NS)

EE-422

Time : 3 Hours

Max. Marks : 100

The candidates shall limit their answers precisely within the answer-book (40 pages) issued to them and no supplementary/continuation sheet will be issued.

Note : Candidates are required to attempt five questions in all selecting one question from each of the sections A, B, C & D of the question paper and all subparts of the questions in Section E. Use of non-programmable calculator is allowed.

SECTION - A

1. (a) Explain in detail the system viewpoint regarding computer aided power system analysis. (10)
- (b) What do you understand by a single line diagram of a power system and what is its importance? How can you construct a single line diagram for a three phase power system network? (10)
2. (a) Derive the expression for Ybus matrix in terms of topology matrices. (10)
- (b) For the transmission network shown in Figure 1, the lines 2-3 have half line charging admittances of $j0.005$ and $j0.01$, respectively in p.u. Write the Ybus matrix by inspection. The shunt capacitor at bus(4) has an admittance $j0.02$. (10)

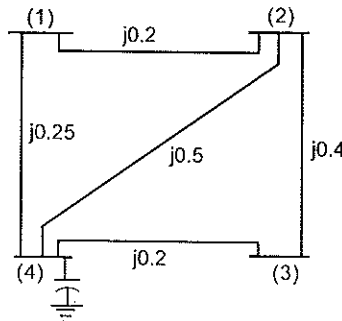


Figure 1

3. Derive the equations for the total fault current in terms of symmetrical components and phase quantities for the following faults at bus p for a general system.
 - (i) Three-phase (not grounded)
 - (ii) line to line
 - (iii) line to line to ground. (20)
4. The positive sequence network of a three bus power system is shown in Figure-2. The three port description of the generator transmission network is given to be

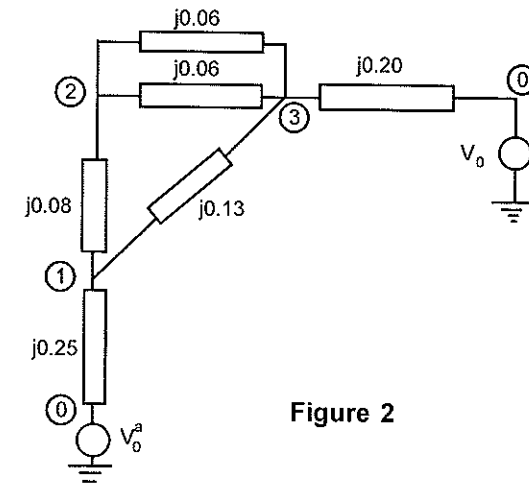


Figure 2

$$\begin{bmatrix} V1 \\ V2 \\ V3 \end{bmatrix} = j \begin{bmatrix} 0.1274 & 0.1061 & 0.0981 \\ 0.1061 & 0.1345 & 0.1151 \\ 0.0981 & 0.1151 & 0.1215 \end{bmatrix} \begin{bmatrix} I1 \\ I2 \\ I3 \end{bmatrix} + \begin{bmatrix} 1 \\ 1 \\ 1 \end{bmatrix} V_0^a$$

For a symmetrical three-phase to ground fault with $Z_F = j0.1$ p.u., find the fault currents for faults at buses 1, 2 and 3. For faults at bus 1, find all the bus voltages and line currents. Assume $V_0^a = 1 + j0$. (20)

SECTION - C

5. What is load flow solution? Explain its significance in power system analysis. (20)
6. Explain clearly with a flow chart the computational procedure for load flow solution using Newton-Raphson method when the system contains all types of buses. (20)

SECTION - D

7. Derive swing equation and discuss its application in study of power system stability. (20)
8. A 50 Hz generator is delivering 50% of the power that it is capable of delivering through a transmission line to an infinite bus. A fault occurs that increases the reactance between the generator and the infinite bus to 500% of the value before the fault. When the fault is isolated, the maximum power that can be delivered is 75% of the original maximum value. Determine the critical clearing angle for the condition described. (20)

SECTION - E

9. (i) What is a single line diagram?
- (ii) What are the components of power system?
- (iii) Define load bus and give its importance.
- (iv) List the factors that affect the transient stability
- (v) State drawbacks of Newton Raphson method.
- (vi) Give applications and limitations of equal area criterion.

- (vii) Give criterion for selection of breakers.
- (viii) What is bus admittance matrix?
- (ix) Give a list of shunt type faults.
- (x) What is optimal ordering? (2×10=20)